


# **Continue - Application of Combinational Logic Circuit / DECODER- ENCODER & Bit Converters**

First Class

# Decoder

- **Decoder** – Is a digital circuit that detects the presence of a specified combination of bits (code) on its input and indicates the presence of that code by a specified output level.
- **Decoding** – Is the conversion of an  $n$ -bit input code to an  $m$ -bit output code with  $n \leq m \leq 2^n$  such that each valid code word produces a unique output code
- Circuits that perform decoding are called *decoders*
- This a 1-to-2 Line decoder – exactly one of the output lines will be active.

A	D <sub>0</sub>	D <sub>1</sub>
0	1	0
1	0	1

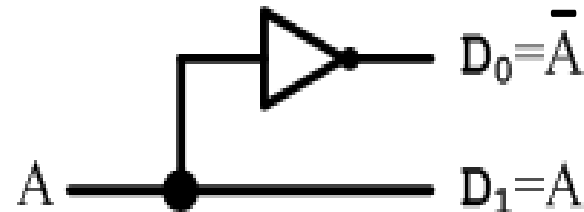


# Decoder

**Example:** Determine the logic required to decode the binary Number **1001** by producing a High level on the output

**Solution:** You must be sure that all of the inputs to the AND gate are HIGH when the binary number 1001 occurs,


$$X = A_3 \bar{A}_2 \bar{A}_1 A_0$$

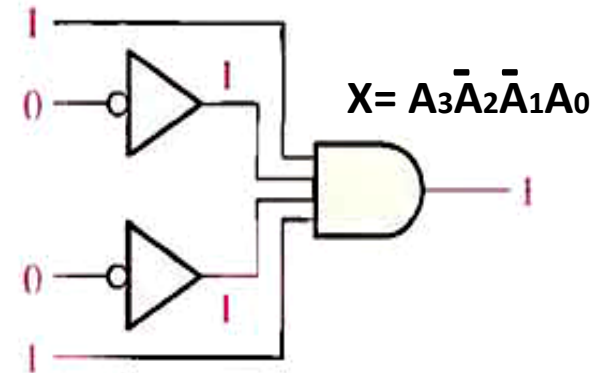

# Decoder

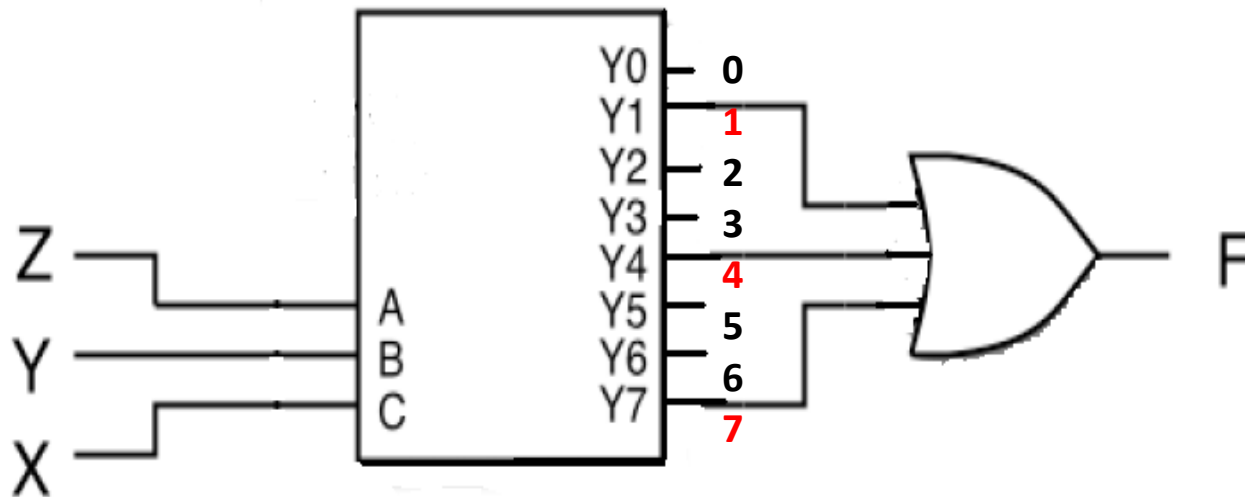- **Example:** Realize  $F(X, Y, Z) = \Sigma(1, 4, 7)$  with a decoder


**Solution:** 1, 4, 7 means the three outputs obtained from eight output.



# Decoder


- A 2-to-4 line decoder

$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

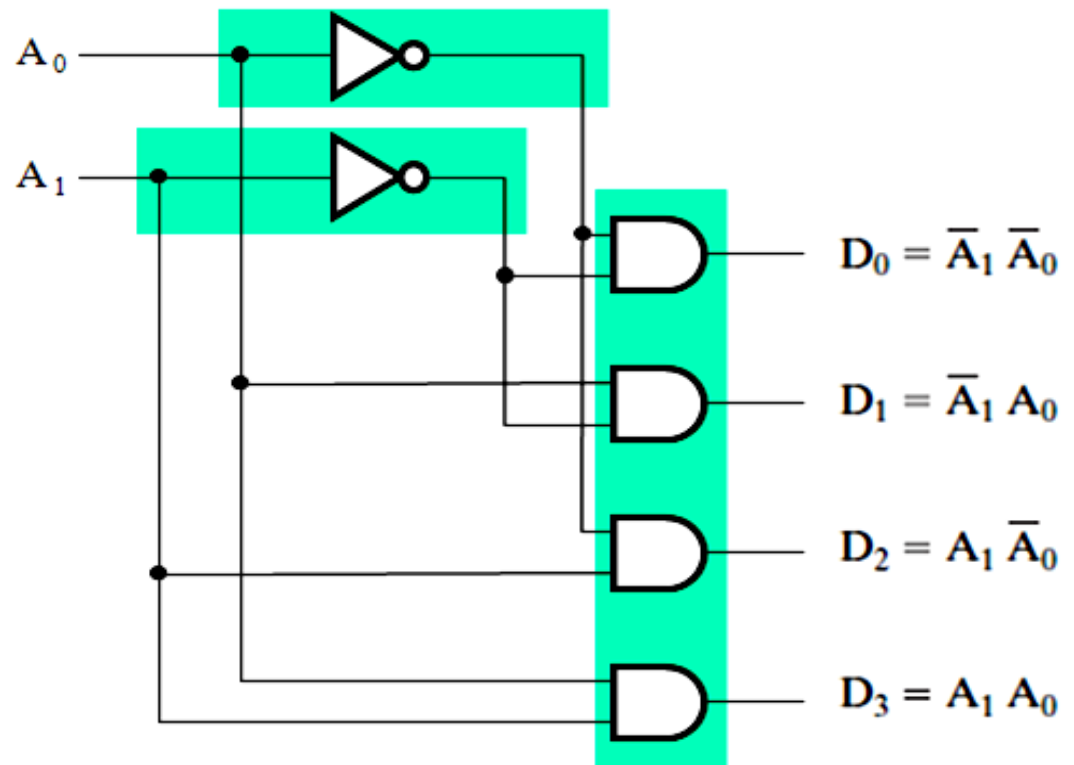


# Decoder

- 2-to-4,
- 3-to-8,
- ...
- n-to- $2^n$

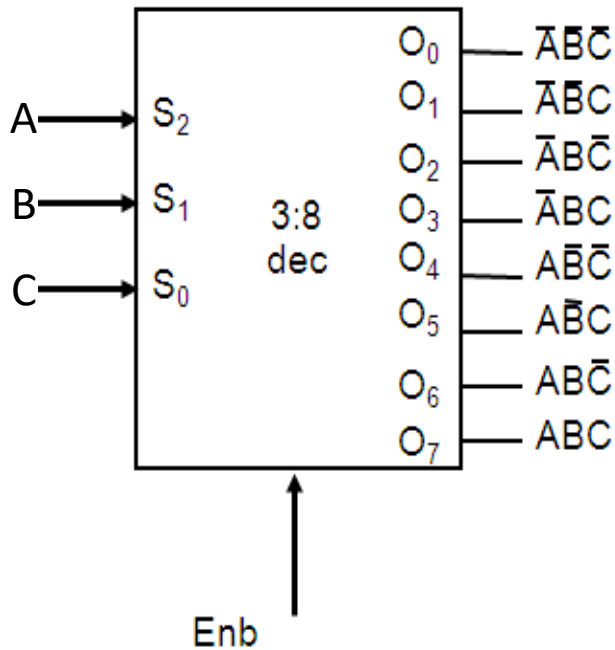

$Enb$	A	B	C	O0	O1	O2	O3	O4	O5	O6	O7
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	1							
1	0	0	1		1						
1	0	1	0			1					
1	0	1	1				1				
1	1	0	0					1			
1	1	0	1						1		
1	1	1	0							1	
1	1	1	1								1

# 3-to-8 Decoder with Enable

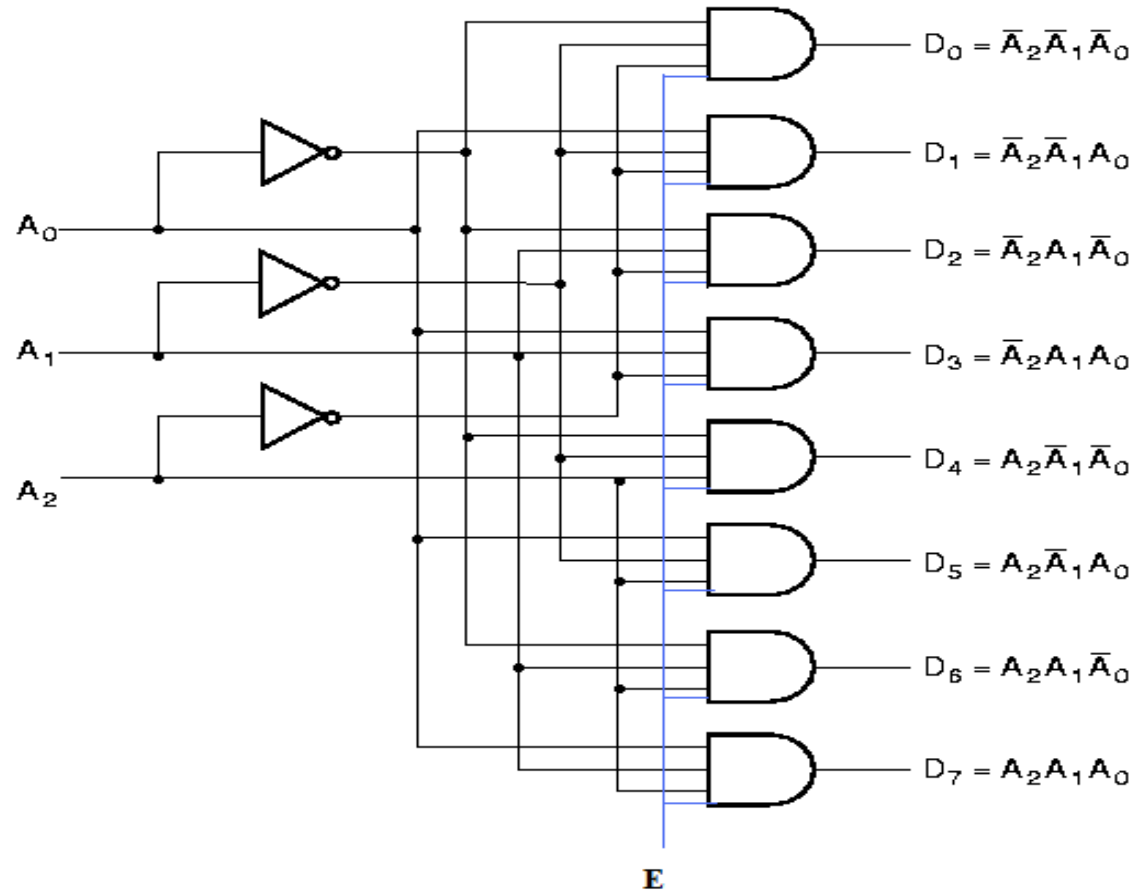

# Application of Decoder

- **Example:** Realize the 1 bit-binary adder circuit using decoder.


**Solution:** The truth table is as shown, so the output function should be:

$$S(X, Y, Z) = \sum m(1, 2, 4, 7)$$

$$C(X, Y, Z) = \sum m(3, 5, 6, 7)$$

**Truth Table for 1-bit Binary Adder**

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

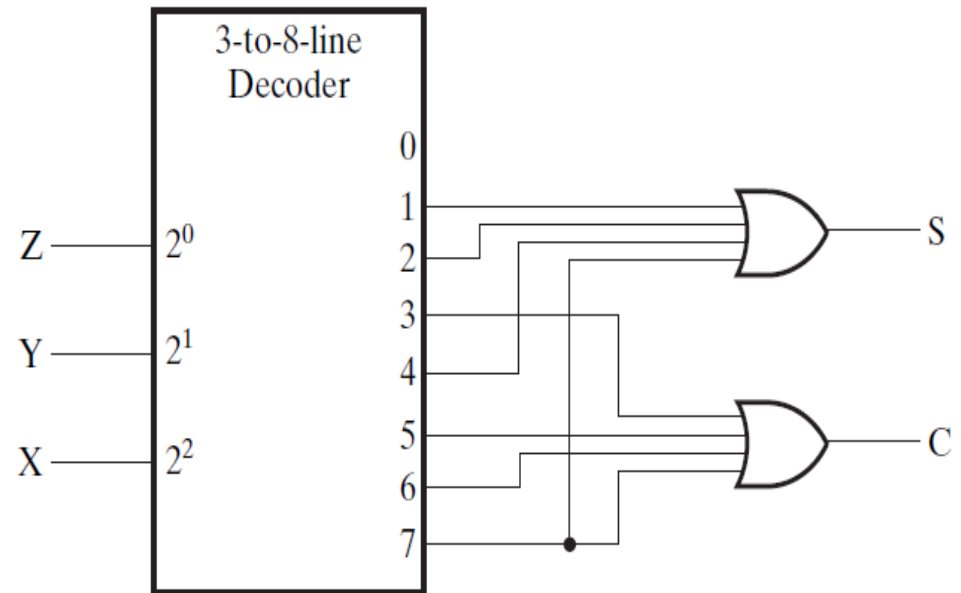



# Application of Decoder

- **Implementing General Logic**

Any combinational circuit can be constructed using decoders and OR gates!

**Example:** design a circuit that can realize the output below:


$$F_1 = A' B C' D + A' B' C D + A B C D$$

$$F_2 = A B C' D' + A B C$$

$$F_3 = (A' + B' + C' + D')$$


Solution:

Note: X' means  $\overline{X}$

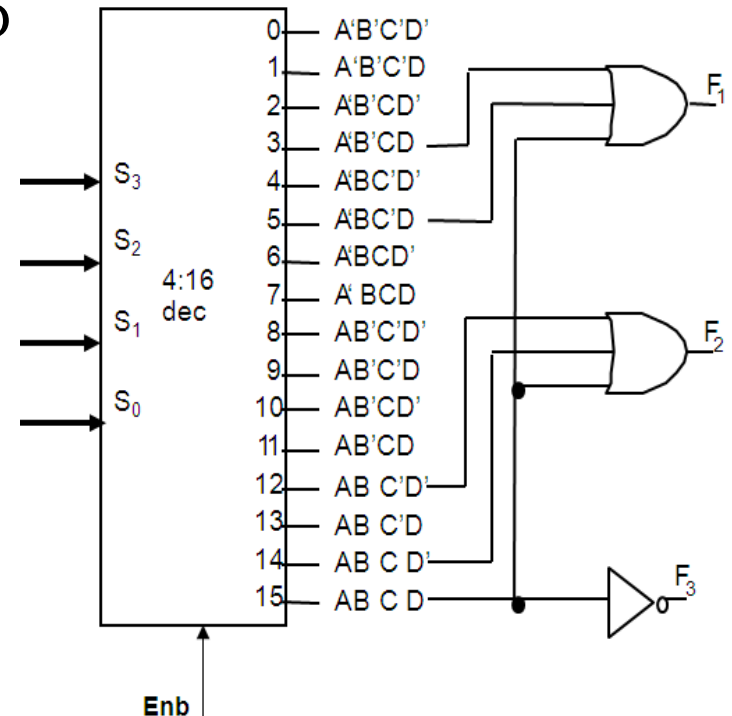
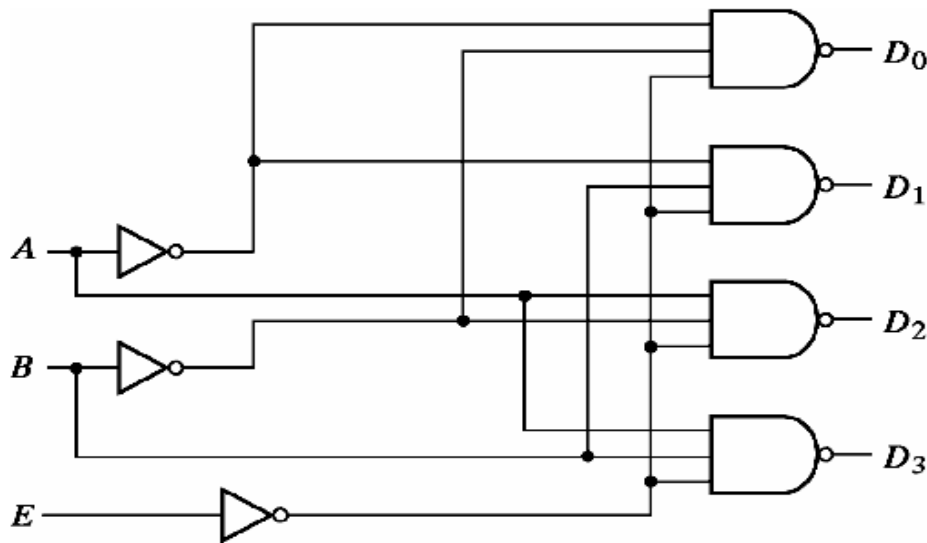
# Active Low Decoder

- If an active-low output is required for each decoded number, the entire decoder can be implemented with NAND gates and inverters.
- **Example:** 2-to-4 Decoder is enabled when  $E=0$  and an output is active if it is 0



(a) Logic diagram


$E$	$A$	$B$	$D_0$	$D_1$	$D_2$	$D_3$
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

# Decoder Expansion

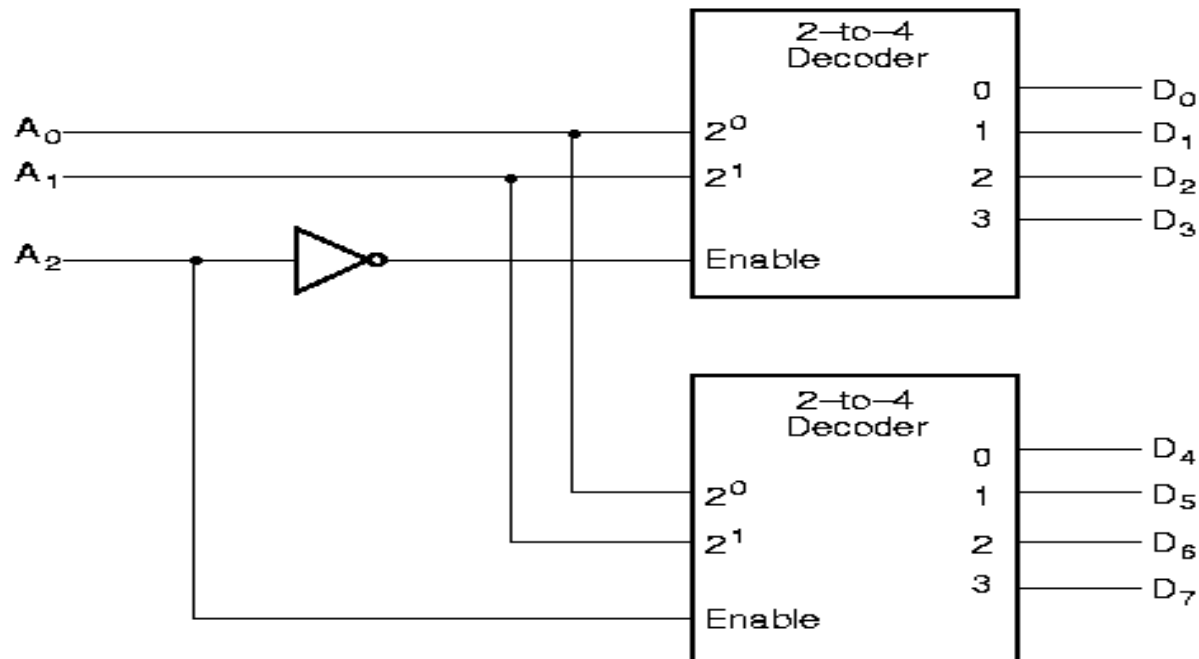
## Decoder expansion

- Combine two or more small decoders with enable inputs to form a larger decoder. 3-to-8-line decoder constructed from two 2-to-4-line decoders
  - **The MSB is connected to the enable inputs**
  - **if  $A_2=0$ , upper is enabled; if  $A_2=1$ , lower is enabled.**




# Combining Two 2-4 Decoders to Form One 3-8 Decoder Using Enable Switch

$A_2$	$A_1$	$A_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

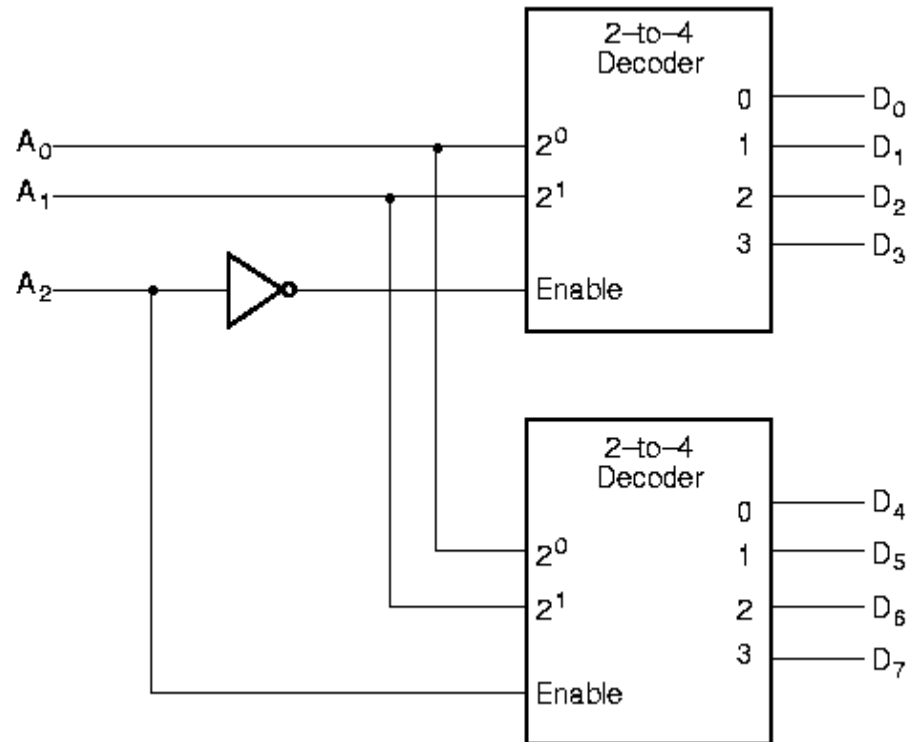

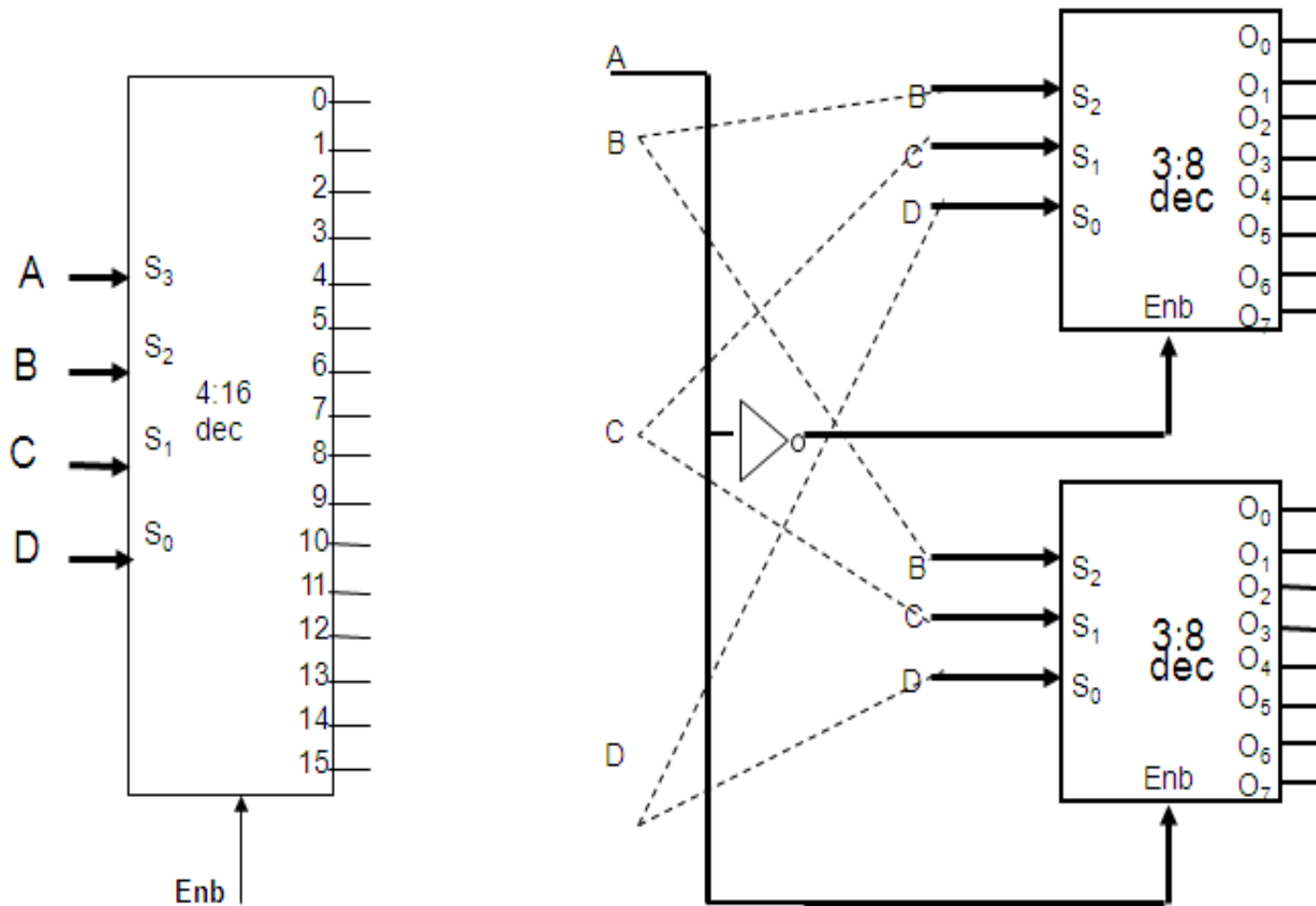
# Combining Two 3-8 Decoders to Form One 4-16 Decoder Using Enable Switch





# 74HC154 Integrated Circuit

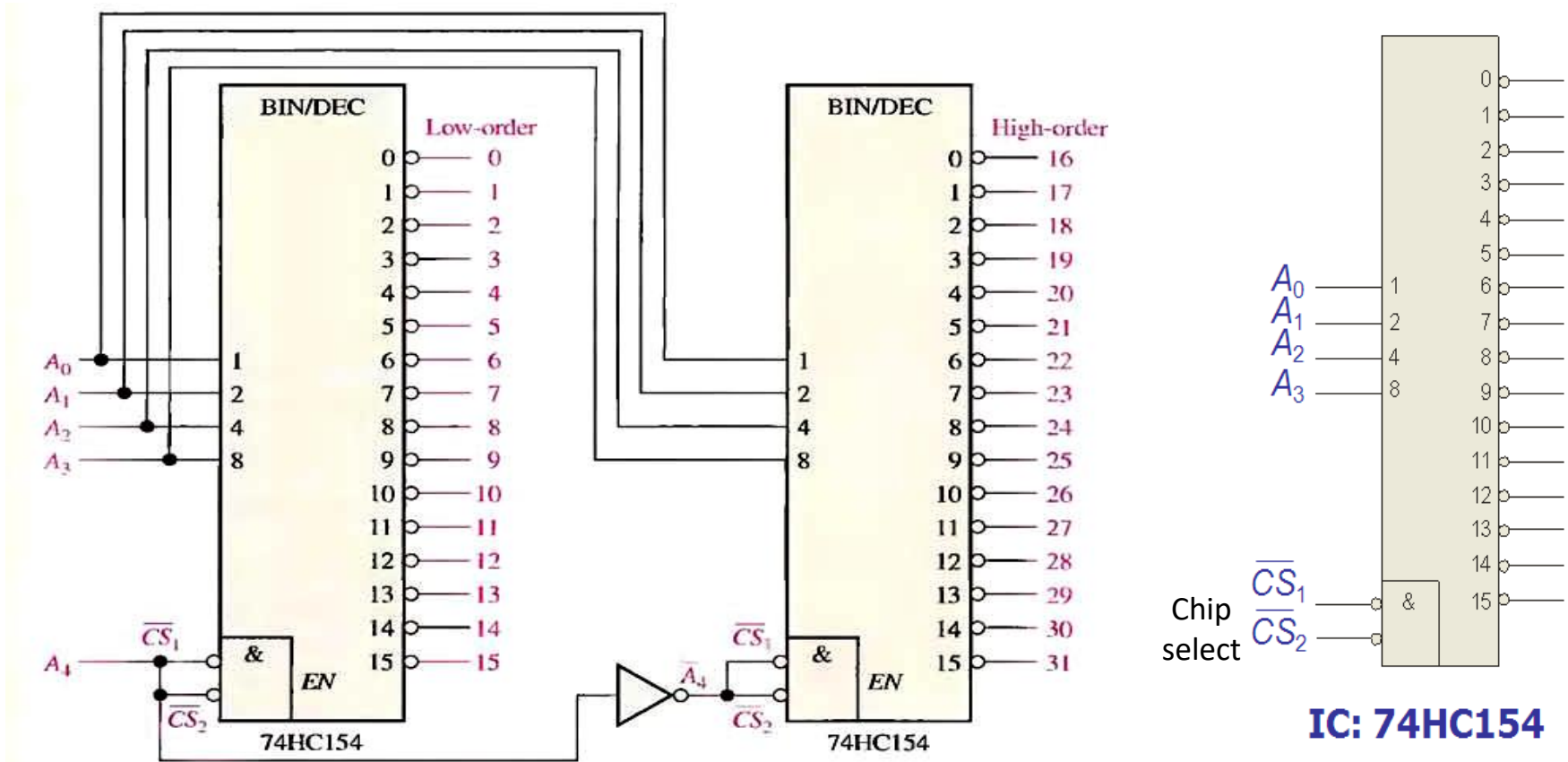- **Example:** A certain application requires that a 5-bit number be decoded. Use a 74HC154 IC decoders to implement the logic.
- **Solution:** Since this IC handle only 4-bits, two decoder must be used.



# Application of Decoder in Computer

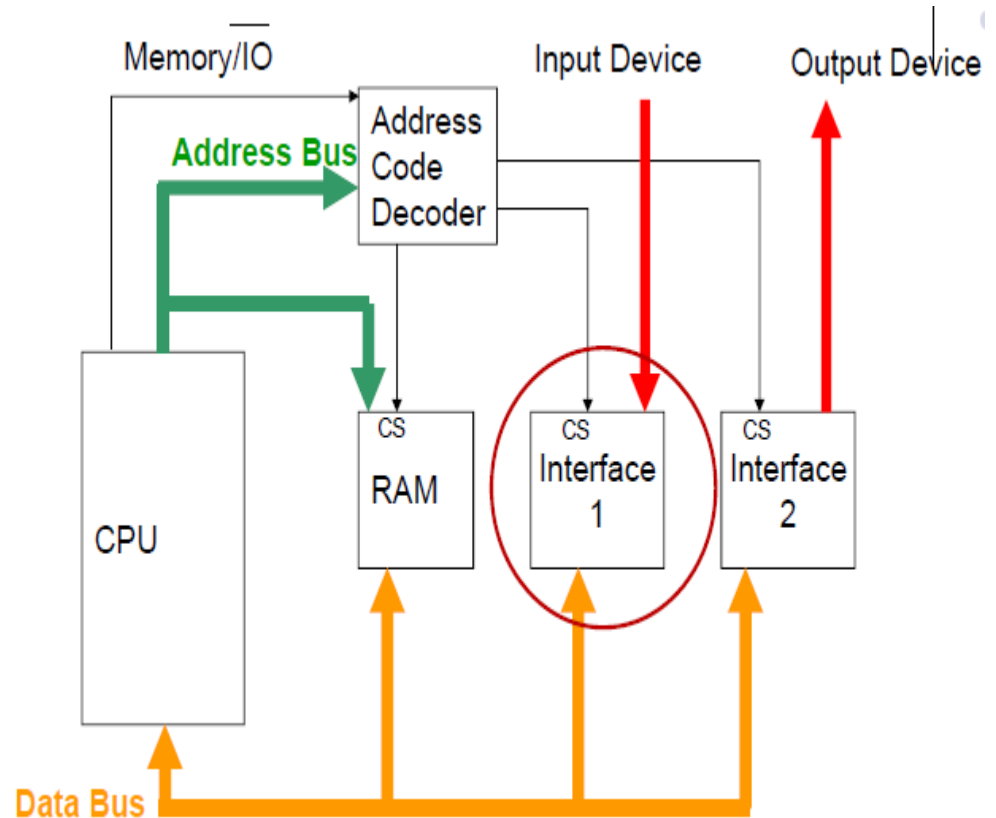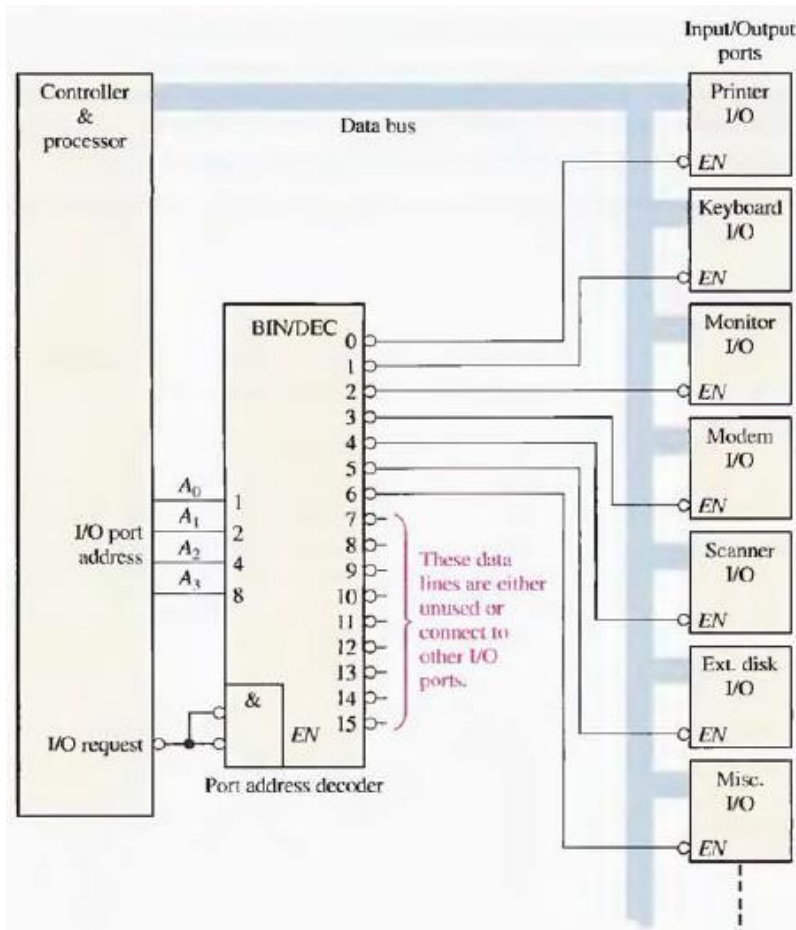

# The BCD to Decimal Decoder



- It convert each BCD (8421 code) into one-to-ten possible decimal digit indications. It is called 4-to-10 line decoder or a 1-to-10 decoder.

DECIMAL DIGIT	BCD CODE				DECODING FUNCTION
	$A_3$	$A_2$	$A_1$	$A_0$	
0	0	0	0	0	$\bar{A}_3\bar{A}_2\bar{A}_1\bar{A}_0$
1	0	0	0	1	$\bar{A}_3\bar{A}_2\bar{A}_1A_0$
2	0	0	1	0	$\bar{A}_3\bar{A}_2A_1\bar{A}_0$
3	0	0	1	1	$\bar{A}_3\bar{A}_2A_1A_0$
4	0	1	0	0	$\bar{A}_3A_2\bar{A}_1\bar{A}_0$
5	0	1	0	1	$\bar{A}_3A_2\bar{A}_1A_0$
6	0	1	1	0	$\bar{A}_3A_2A_1\bar{A}_0$
7	0	1	1	1	$\bar{A}_3A_2A_1A_0$
8	1	0	0	0	$A_3\bar{A}_2\bar{A}_1\bar{A}_0$
9	1	0	0	1	$A_3\bar{A}_2\bar{A}_1A_0$




# The BCD to Decimal Decoder

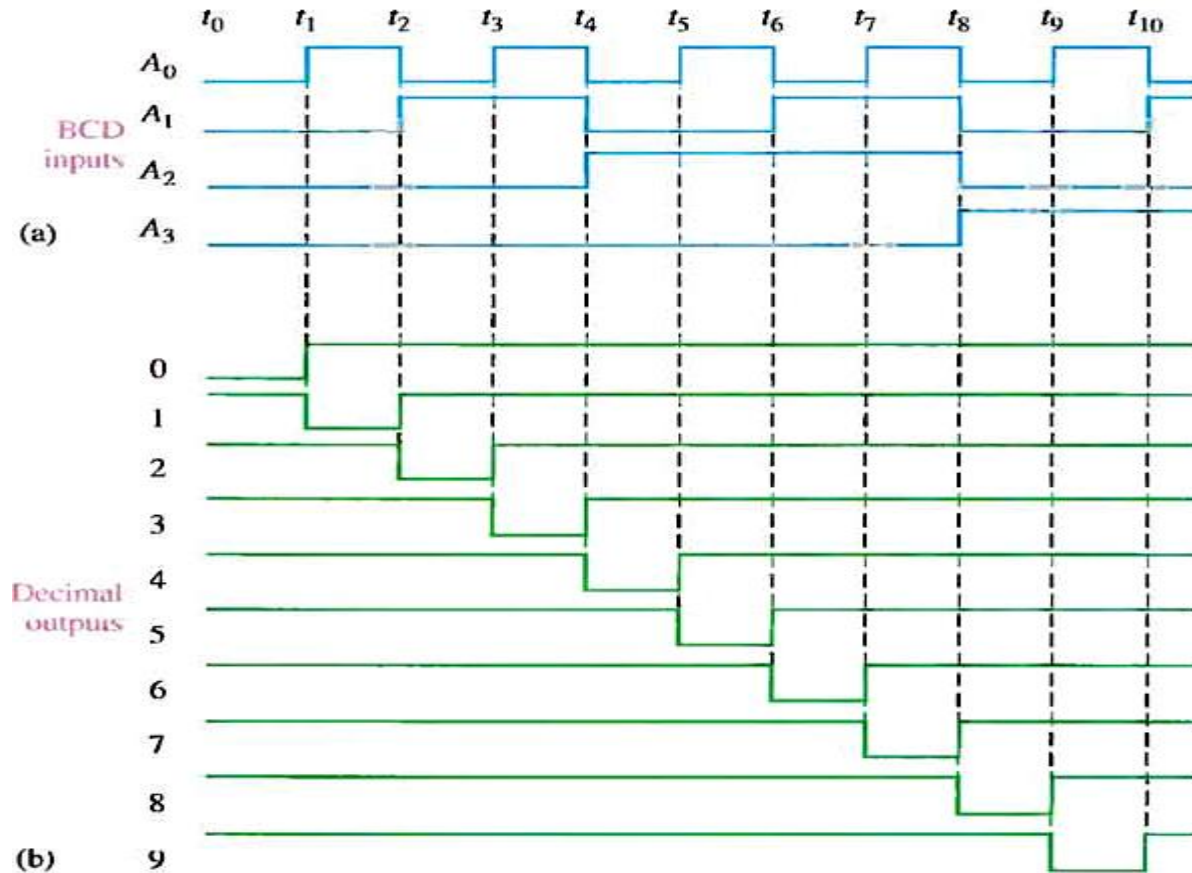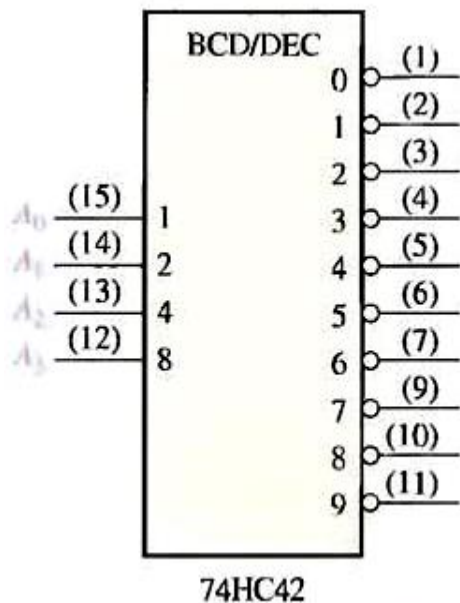- Example: the 74HC42 is an IC BCD-to-decimal decoder. If the input waveforms as in Fig. are applied to the IC inputs, show the output waveforms.



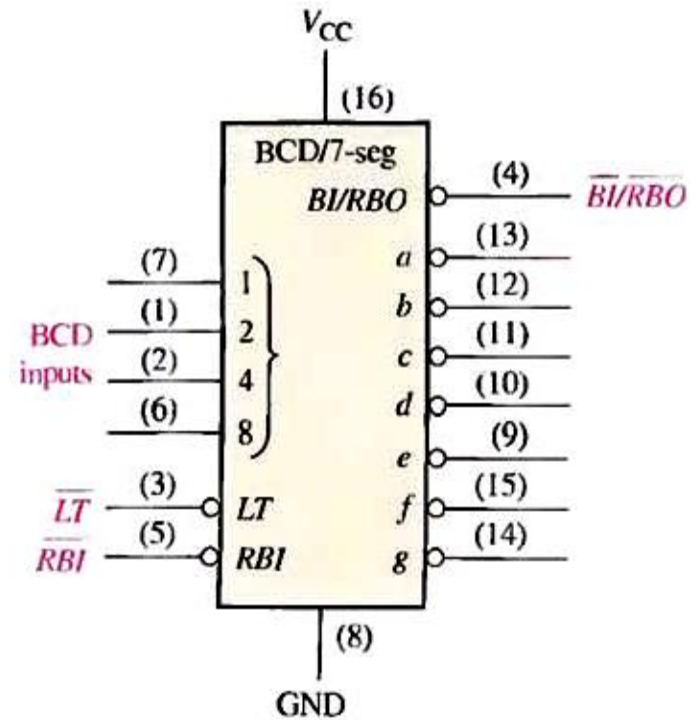
# The BCD to 7-Segment Decoder

- This decoder accept the BCD code on its input and provides outputs to drive 7-segment display devices to produce a decimal readout.
- As an example, the 74LS47 . LT (Lamp Test), RBI (Ripple Blanking Input), BI/RBO (Blanking Input/ Ripple Blanking Output). All output are non-active (HIGH) if (0000) is on inputs and if RBI is low. This causes the display to be blank and produces a LOW RBO.



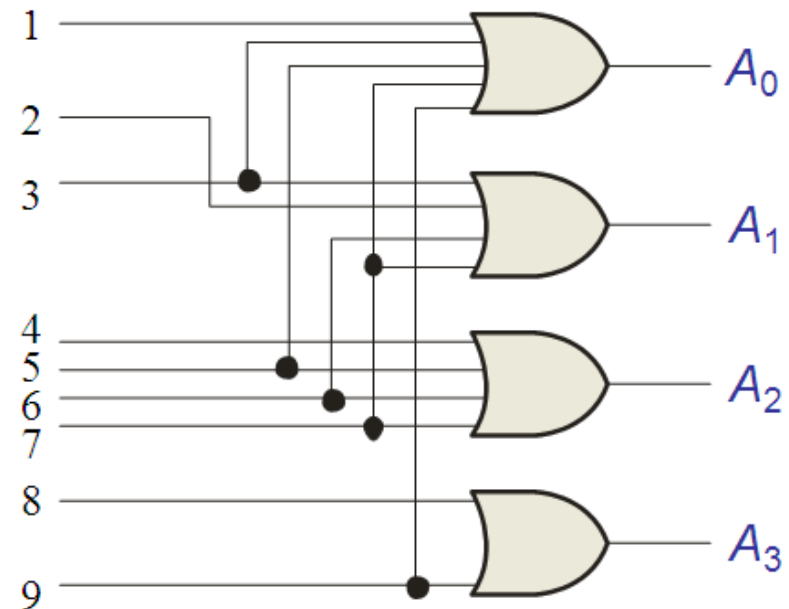
# Encoder

- An encoder is a combinational logic cct. that essentially performs a reverse decoder function. It is accepts an active logic level on one of its inputs representing a digit, such as a decimal or octal digits, and converts it to a coded output, such as BCD or binary.
- IC: 74HC147 16-to-4 encoder (decimal-to-BCD)
- IC: 74F148 8-to-3 encoder



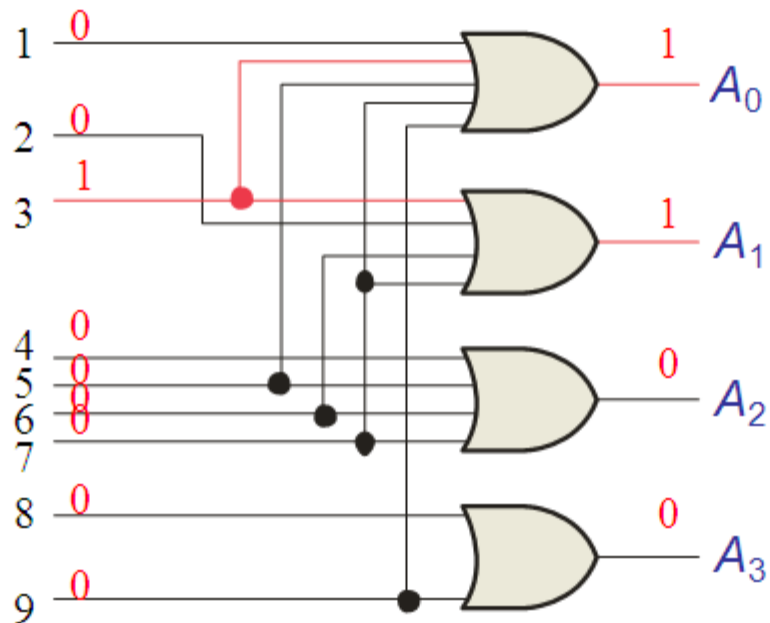
# Encoder

Show how the decimal-to-BCD encoder converts the decimal number 3 into a BCD 0011.


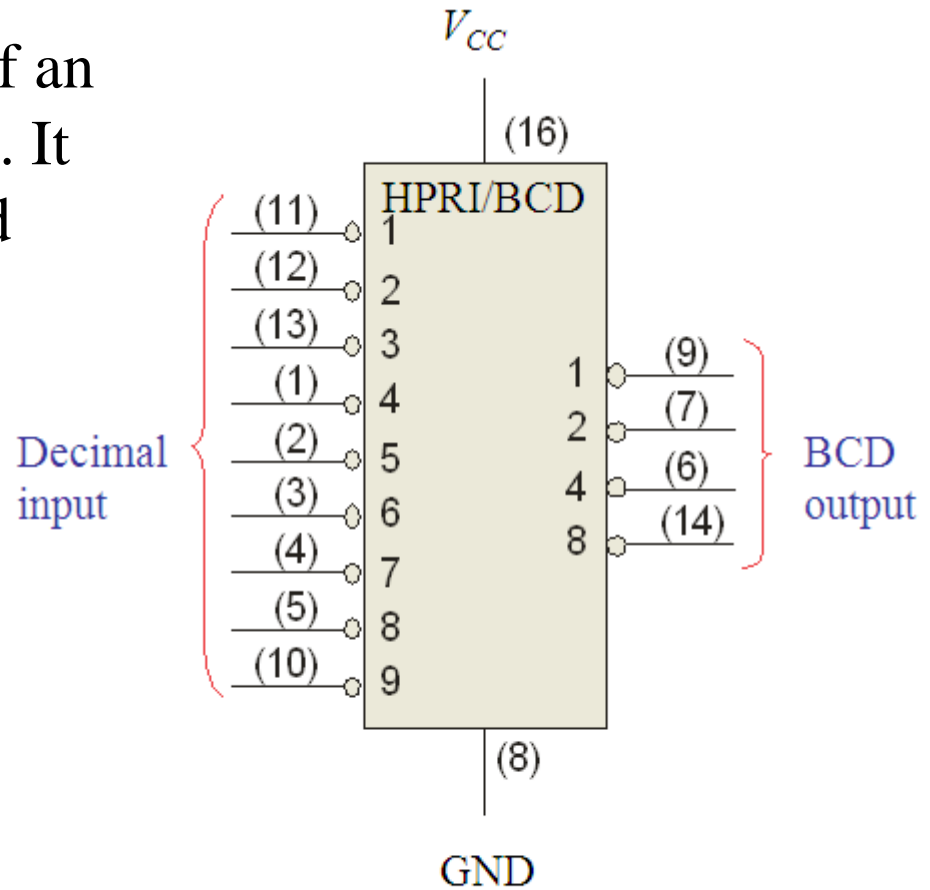
# Encoder



The 74HC147 is an example of an IC encoder (Decimal-to-BCD). It has ten active-LOW inputs and converts the active input to an active-LOW BCD output.



74HC147

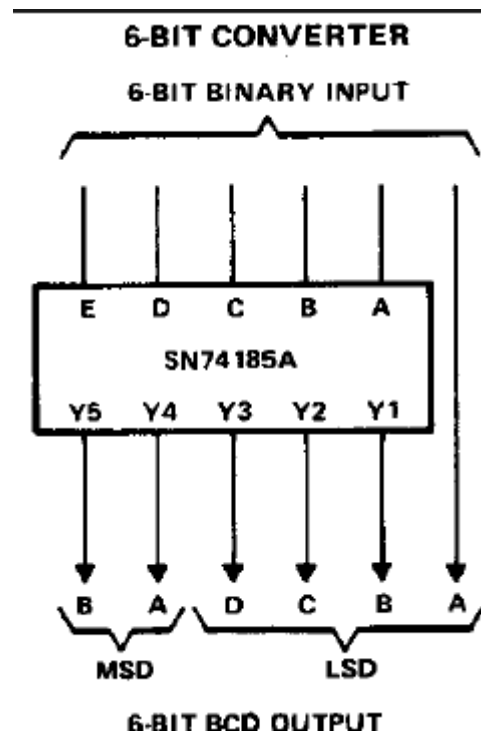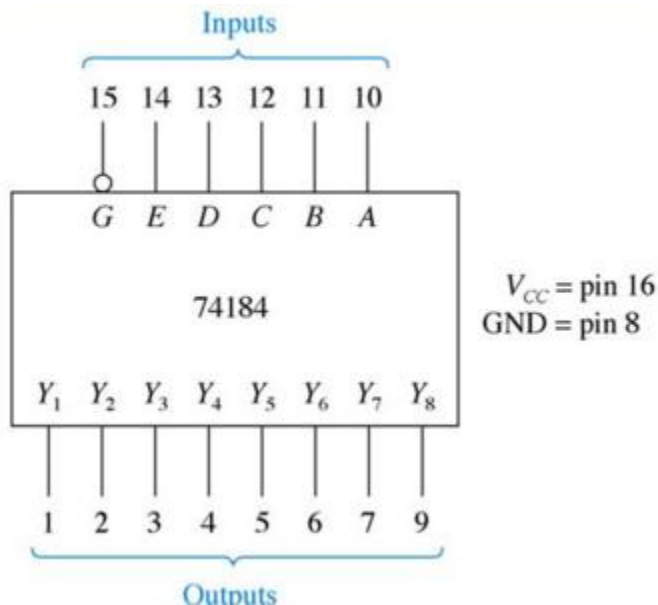
# Code Converters

- BCD-to-Binary Conversion
- IC: 74184
- Binary-to-BCD Conversion
- IC: 74185



# Code Converters

## ■ BIN-to-Gray

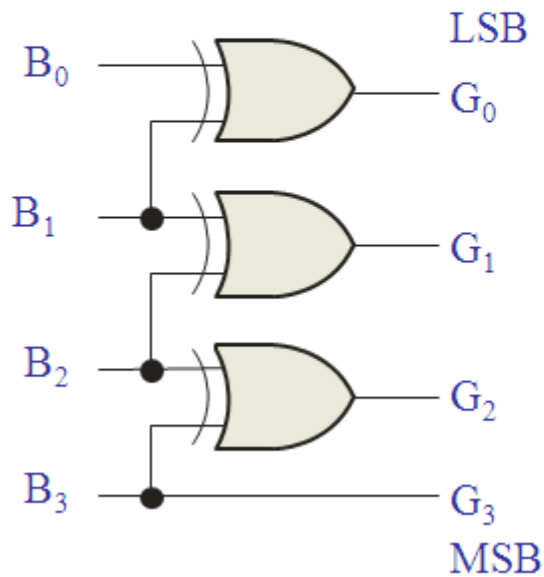

## ■ Gray-to-BIN

